


Universidade Federal do Rio Grande do Sul  
Instituto de Informática  
Departamento de Informática Aplicada  
INF01175 – Sistemas Digitais para Computação

**Trabalho 1**  
**Somador e Subtrator 4bits**


Cássio Miguel Entrudo

Porto Alegre, 10 de outubro de 2017

Imagem do testbench contendo todos os sinais importantes:

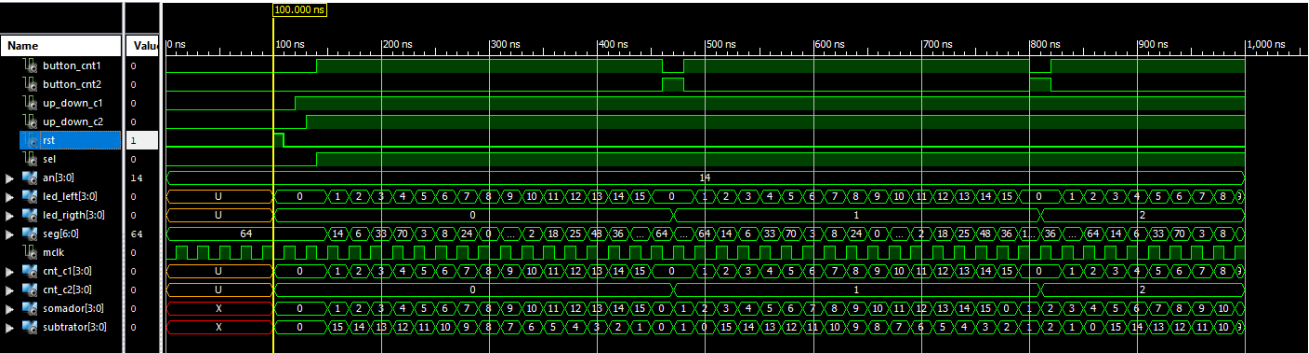

 Aqui podemos verificar os contadores cnt\_1 e cnt\_2 e os registradores somador e subtrator alterando seus valores a cada borda de clock.



Informações:

Device Utilization Summary				
Logic Utilization	Used	Available	Utilization	Note(s)
Number of Slice Flip Flops	24	1,920	1%	
Number of 4 input LUTs	32	1,920	1%	
Number of occupied Slices	27	960	2%	
Number of Slices containing only related logic	27	27	100%	
Number of Slices containing unrelated logic	0	27	0%	
Total Number of 4 input LUTs	33	1,920	1%	
Number used as logic	32			
Number used as a route-thru	1			
Number of bonded IOBs	26	83	31%	
Number of BUFMUXs	1	24	4%	
Average Fanout of Non-Clock Nets	3.20			

```

Found 16x7-bit ROM for signal <saida_7bits>.
Found 4-bit updown counter for signal <cnt_c1>.
Found 4-bit updown counter for signal <cnt_c2>.
Found 8-bit register for signal <reg1>.
Found 8-bit register for signal <reg2>.
Found 4-bit subtractor for signal <subtrator>.
Summary:
inferred   1 ROM(s).
inferred   2 Counter(s).
inferred  16 D-type flip-flop(s).
inferred   1 Adder/Subtractor(s).
Unit <trabalhol> synthesized.

```

```

=====
HDL Synthesis Report

```

```

Macro Statistics
# ROMs                                     : 1
  16x7-bit ROM                             : 1
# Adders/Subtractors                       : 1
  4-bit subtractor                         : 1
# Counters                                 : 2
  4-bit updown counter                     : 2
# Registers                                : 16
  1-bit register                           : 16

```

```

=====
Advanced HDL Synthesis Report

```

```

Macro Statistics
# ROMs                                     : 1
  16x7-bit ROM                             : 1
# Adders/Subtractors                       : 1
  4-bit subtractor                         : 1
# Counters                                 : 2
  4-bit updown counter                     : 2
# Registers                                : 16
  Flip-Flops                               : 16

```

```
=====
*                               Final Report                               *
=====
```

Clock Information:

Minimum period: 4.262ns (Maximum Frequency: 234.632MHz)  
Minimum input arrival time before clock: 3.819ns  
Maximum output required time after clock: 10.083ns  
Maximum combinational path delay: 8.330ns

```
=====
```

Design Summary:

Number of errors: 0  
Number of warnings: 0

Logic Utilization:

Number of Slice Flip Flops:	24 out of	1,920	1%
Number of 4 input LUTs:	32 out of	1,920	1%

Logic Distribution:

Number of occupied Slices:	27 out of	960	2%
Number of Slices containing only related logic:	27 out of	27	100%
Number of Slices containing unrelated logic:	0 out of	27	0%

\*See NOTES below for an explanation of the effects of unrelated logic.

Total Number of 4 input LUTs:	33 out of	1,920	1%
Number used as logic:	32		
Number used as a route-thru:	1		